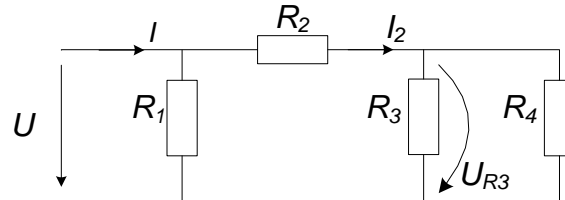



Resistors. Ohm's Law

1-1 For the circuit below we know: $R_1=10\Omega$, $R_2=9\Omega$, $R_3=15\Omega$, $R_4=10\Omega$ and supplying voltage $U=60V$. Calculate: a) the equivalent resistance regarding the supplying terminals, R_e ; b) the total current absorbed by the resistances, I ; c) the current through the resistance R_2 , I_2 ; d) the voltage on the resistance R_3 , U_{R3} ; the power dissipated in the resistance R_4 , P_{R4} .




Problem 1-8

1-2 Find the value of the equivalent resistance, R_{eq} , between terminals a and b, for the sub-circuit shown below.

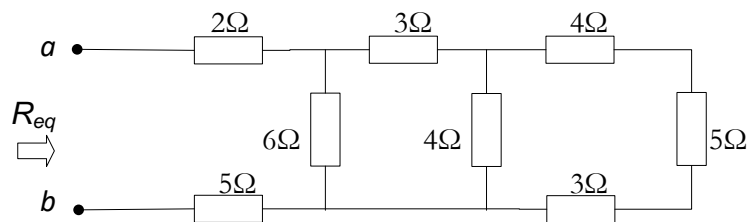


Problem 1-13

1-3 Determine the current I_s generated by the current source in the circuit below if the power dissipated in the 2Ω s resistance is $32W$.

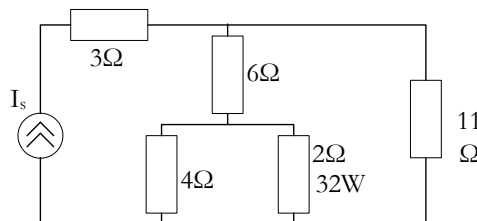


Problem 1-17

1-4 Determine the voltage E generated by the voltage source in the circuit below if the current flow to the 3Ω s resistance is $I_0=4A$.

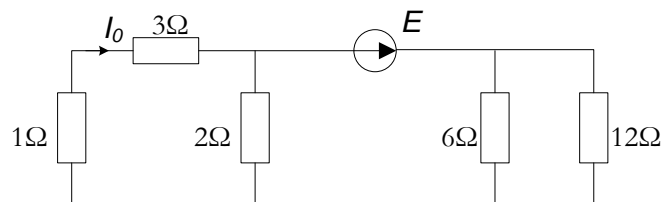

Problem 1-18


1-5 Determine the current I_s generated by the current source in the circuit below if the voltage drop on the 2Ω s resistance is $4V$.

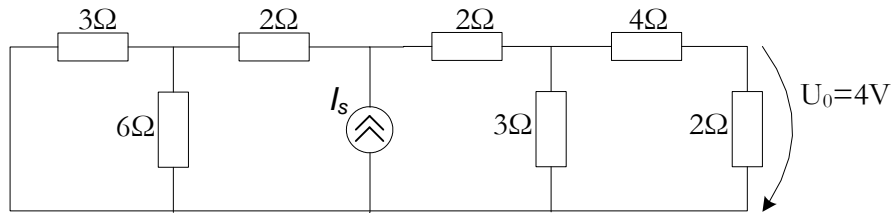

Problem 1-21


Kirchhoff's Laws

2-1 For the circuit below we know: $R_1=5\Omega$, $R_2=10\Omega$, $R_3=6\Omega$, $R_4=3\Omega$, $R_5=2\Omega$, $E_1=10V$, $E_2=5V$, $E_5=5V$. Identify the number of nodes and circuit branches and calculate the branch currents using: a) the Kirchhoff Laws; b) the nodal analysis; c) the mesh analysis. Calculate the generated and removed power in the circuit and verify the power conservation theorem.

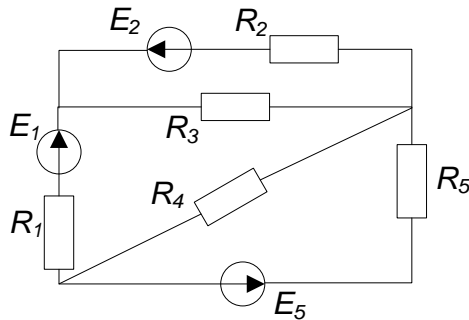


Problem 2-1

2-2 Find the currents I_1 , I_2 , I_3 for the circuit below and verify the power conservation theorem.

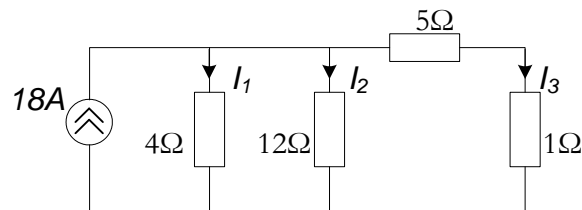


Problem 2-4

2-3 For the circuit below calculate the dissipated power in the 8Ω 's resistance.

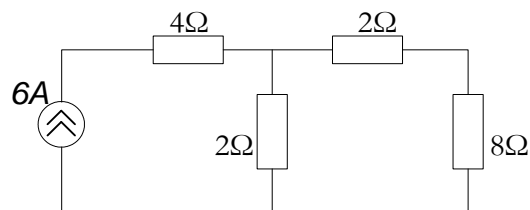


Problem 2-5

2-4 Find the currents I , I_0 , I_1 for the circuit below and verify the power conservation theorem.

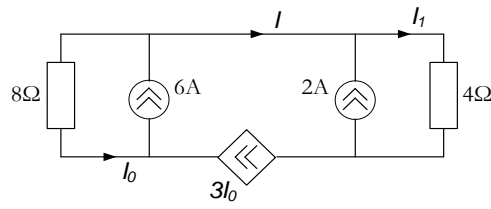


Problem 2-6

2-5 Find the currents I_1 , I_2 , I_3 for the circuit below and verify the power conservation theorem.

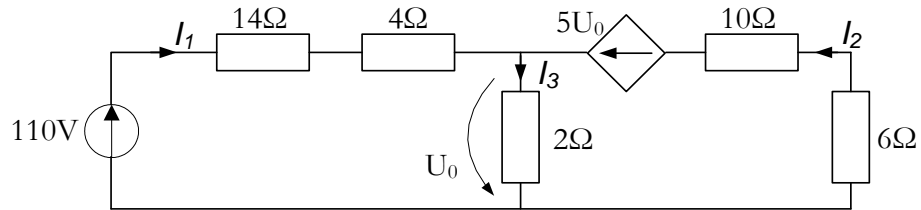


Problem 2-7

2-6 Find the currents I_1 for the circuit below and verify the power conservation theorem.

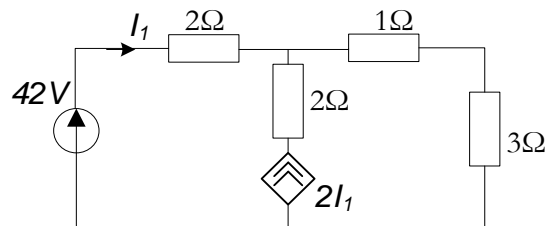


Problem 2-9

2-7 Find the currents I_x for the circuit below and verify the power conservation theorem.

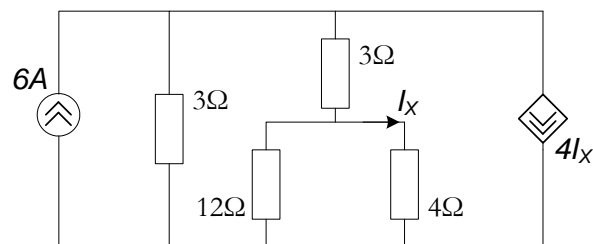


Problem 2-10

2-8 Find the currents I_0 , I_1 , I_2 , I_3 , I for the circuit below and verify the power conservation theorem.

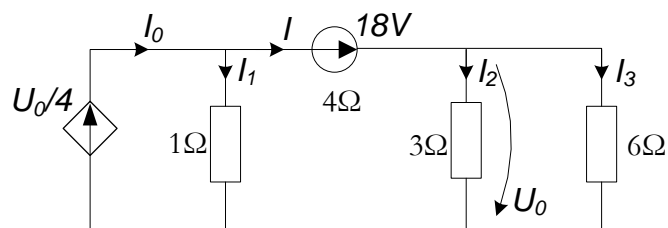


Problem 2-14

2-9 Suppress all the sources in the circuit below and calculate the equivalent resistance, R_{eq} , regarding to the terminals a and b .

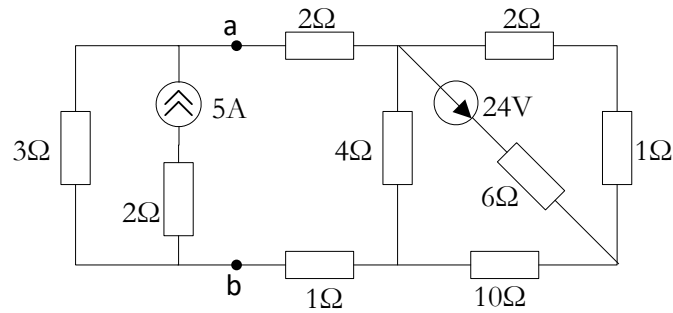


Problem 2-16

2-10 Suppress all the sources in the circuit below and calculate the equivalent resistance, R_{eq} , regarding to the terminals a and b .

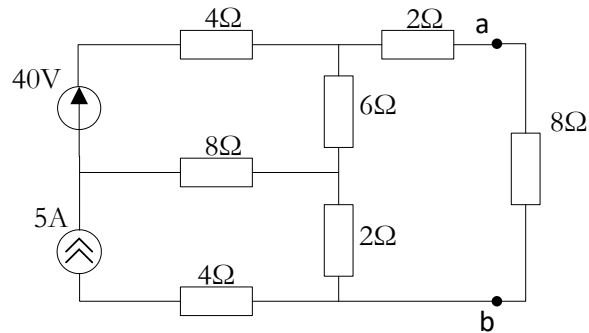

Problem 2-17


2-11 Suppress all the sources in the circuit below and calculate the equivalent resistance, R_{eq} , regarding to the terminals a and b .

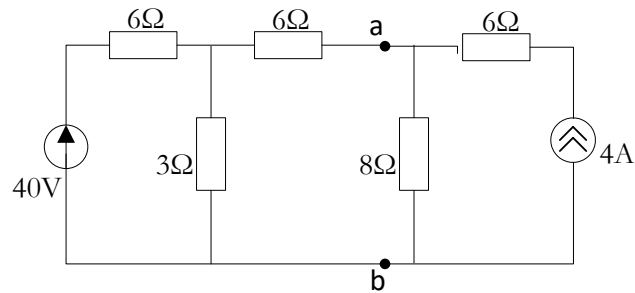

Problem 2-19


Thevenin's and Norton's Theorem

2-12 Determine the Thevenin equivalent circuit (R_{eq} , U_0), viewed by the 10Ω s resistance (terminals a and b) for the circuit below. Find the current I through the 10Ω s resistance.

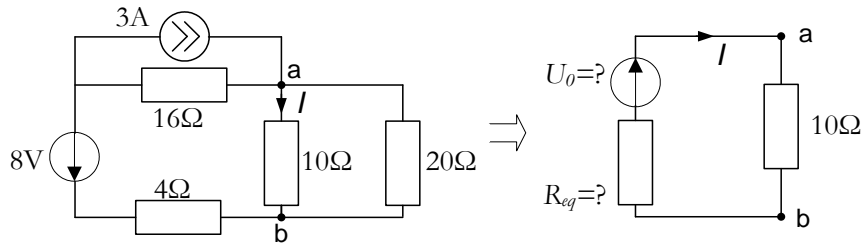


Problem 2-23

2-13 Determine the Thevenin equivalent circuit (R_{eq} , U_0), viewed by the 1Ω s resistance (terminals a and b) for the circuit below. Find the current I through the 1Ω s resistance.

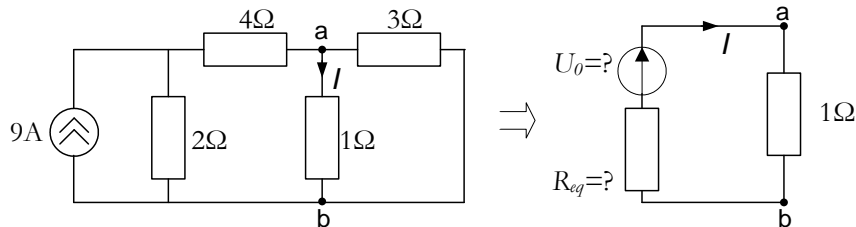

Problem 2-24


2-14 Determine the Thevenin equivalent circuit (R_{eq} , U_0), viewed by the 3Ω s resistance (terminals a and b) for the circuit below. Find the current I through the 3Ω s resistance.

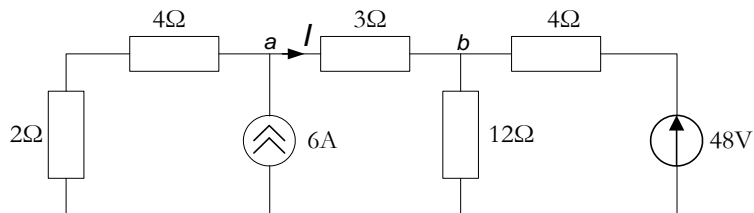

Problem 2-25


Nodal and Mesh Analysis

2-15 For the circuit below, use the nodal analysis to calculate the potential of the nodes. Find the currents in the circuit. The circuit parameters are: $R_1 = R_4 = 4\Omega$, $R_2 = 2\Omega$, $R_3 = 6\Omega$, $R_5 = 3\Omega$, $R_s = 10\Omega$, $E_1 = E_3 = 6V$, $E_4 = 3V$, $E_5 = 4V$, $I_s = 2A$.

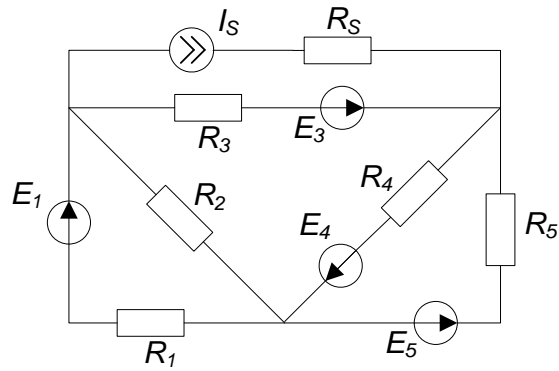


Problem 2-31

2-16 For the circuit below, use the nodal analysis to calculate the potential of the nodes. Find the currents in the circuit.

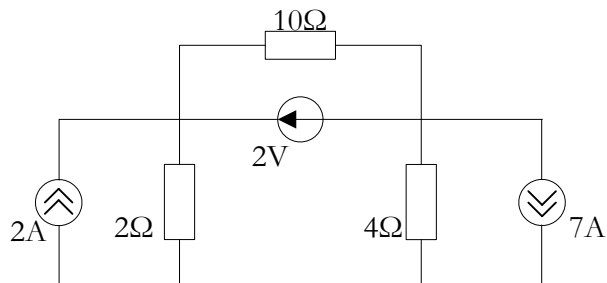


Problem 2-32

2-17 For the circuit below, calculate the voltage U using: a) Norton's theorem; b) the nodal analysis. Calculate the current I using Thevenin's theorem.

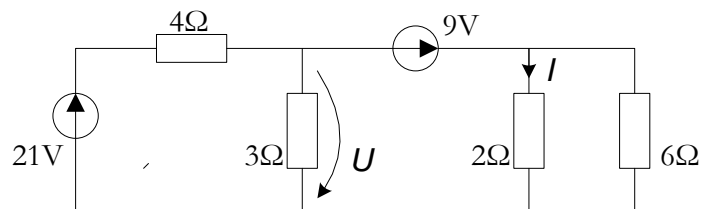


Problem 2-35

2-18 For the circuit below, calculate the currents through the circuit using: a) the Kirchhoff laws; b) the nodal analysis; c) the mesh analysis. Verify the current I by using Thevenin's theorem. Verify the power conservation theorem.

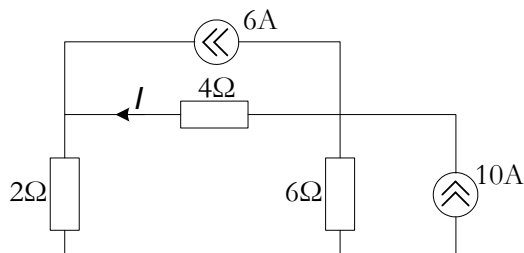


Problem 2-36

2-19 For the circuit below, use the mesh analysis to find the currents in the circuit.

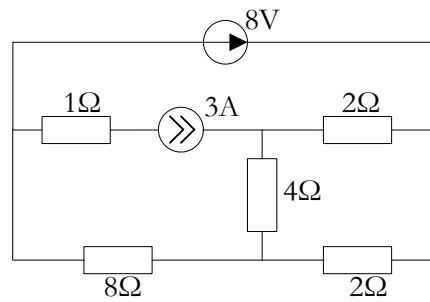

Problem 2-39

2-20 For the circuit below, determine the value of the resistance R which will absorb the greatest power from the circuit.

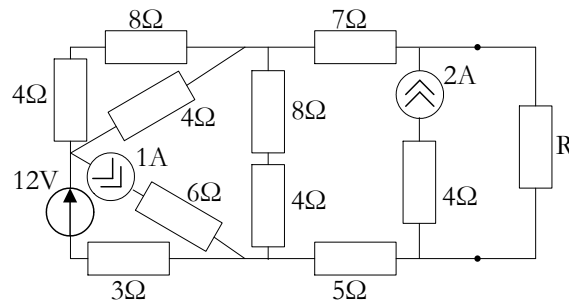

Problem 2-41